



Faculty of Computing and Technology

Department of Computing

Bachelor of Science (Hons) in Computer Science & Software Engineering

End - Semester Examination

Year 2023, Semester 01 -Batch 01

CS/SE 1104– Computer Architecture and Organization

Duration: 02 Hours

Instructions to the candidates:

1. Answer the all the questions.
2. Clearly write the all the calculations where they needed.
3. The total number of marks allocated will be 100.

Question 1

Since humans use decimal notation and computers use binary notation, number conversion is of paramount importance to how computers represent numbers.

- a) Using the following numbers (show all your working): (06 Marks)
- I. 1356, show how a decimal number can be converted to binary.
 - II. 1011100111, show how a different binary number can be converted to decimal.
- b) Using the following numbers (show all your working without going via decimal): (06 Marks)
- I. 1011111000, show how a binary number can be converted to octal.
 - II. 1110001111, show how a binary number can be converted to hexadecimal.

- c) Explain why it is important that, when using the methods described in part (b), the conversion starts at the least significant bit? (04 Marks)
- d) Convert 192.168 to binary. (03 Marks)
- e) Draw a logic circuit for the following functions: (06 Marks)
- I. $F(X, Y, Z) = XY' + XZ' + YZ$
- II. $F(X, Y, Z) = (X + Y')(X' + Z')(Y + Z)$
- [Total 25 Marks]

Question 02

- a) Explain and differentiate between physical, virtual, and logical memory. (06 Marks)
- b) Why is main memory not suitable for permanent program storage or backup purposes? (03 Marks)
- c) Combinational logic can be used to build several computer circuits relating to maths. (06 Marks)
- A key device needed for computational functions is a full adder. Describe from first principles how to build a full adder which adds two-bits and a carry.
- d) Another useful circuit is a shift register. Using D-type flip flops show how to build a four-bit shift register and explain how it works. There is no need to show the individual gates inside the D-type flip flops. (06 Marks)
- e) What do the terms "8-bit" microprocessor, or "32-bit" microprocessor mean? (04 Marks)

[Total 25 Marks]

Question 03

- a) With the aid of a diagram, explain the operation of a computer's CPU at the level of registers, functional units, and buses. (03 Marks)
- You must provide a diagram of the structure of a computer and explain how an instruction is executed in terms of the flow of information between registers and functional units.
- b) Generate the function F for the following K-maps: (10 Marks)

		Y'		Y	
X	Y	00	01	11	10
	m	m0	m1	m3	m2
X'	0	1	0	1	1
X	1	1	1	0	1
		Z'		Z	Z'

I.

		Y'		Y	
W	YZ	00	01	11	10
	m	m0	m1	m3	m2
W'	00	1			1
W'	01	1			1
W	11	1			1
W	10	1			1
		Z'		Z	Z'

II.

- c) Simplify the following functions where D is a don't care function:

(12 Marks)

I. $F(X, Y, Z) = \sum(0, 3, 4)$
 $D(X, Y, Z) = \sum(2, 6)$

II. $F(W, X, Y, Z) = \sum(0, 1, 3, 5, 9, 11)$
 $D(W, X, Y, Z) = \sum(2, 4, 8, 10)$

[Total 25 Marks]

Question 04

All digital systems are constructed from two types of components: combinational logic element (i.e. gates) and sequential elements (i.e. flip flops).

- a) Describe the fundamental difference between these TWO circuit elements and explain why both types are needed to construct a digital computer. (05 Marks)
- b) Explain the difference between the following flip-flops: (06 Marks)

- I. D flip-flop;
- II. JK flip-flop;

c) Show how flip-flops can be used to construct EITHER: (04 Marks)

- I. a shift right register; or
- II. a binary counter.

Construct only ONE of these circuits.

d) Complete the following table for T flip-flop. (10 Marks)

T	$Q(t)$ present output	$Q(t + 1)$ next output
0	0	
0	1	
1	0	
1	1	

[Total 25 Marks]

***** End Paper *****